


10-30 微電子學

圖10.18為理想的串串迴授放大器及等效電路

A：單一方向（由輸入到輸出）傳送的互導放大器

β ：單一方向（由輸出到輸入）傳送的迴授網路


(2) 求 R_{if} :

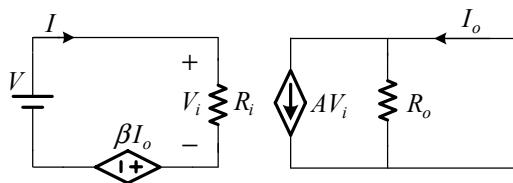

$$V = V_i + \beta I_o = V_i + \beta(AV_i) = (1 + \beta A)V_i$$

$$= (1 + \beta A)I \cdot R_i \quad , \quad \text{得} \quad R_{if} = \frac{V}{I} = R_i \cdot (1 + \beta A)$$


(3) 求 R_{of} :

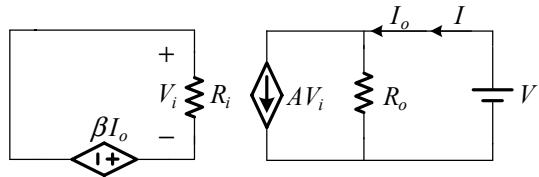


$$I = \frac{V}{R_o} + A V_i = \frac{V}{R_o} + A(-\beta I)$$

$$\Rightarrow (1 + \beta A)I = \frac{V}{R_o} \Rightarrow R_{of} = \frac{V}{I} = R_o(1 + \beta A)$$

二、實際串串回授放大器分析

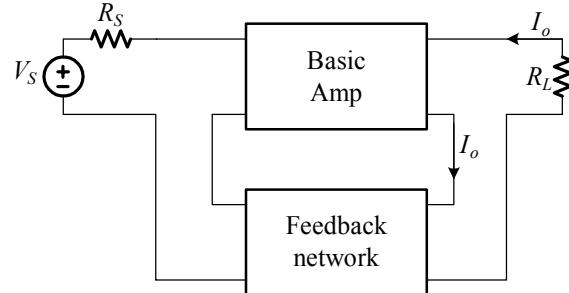


(a)串串回授方塊圖

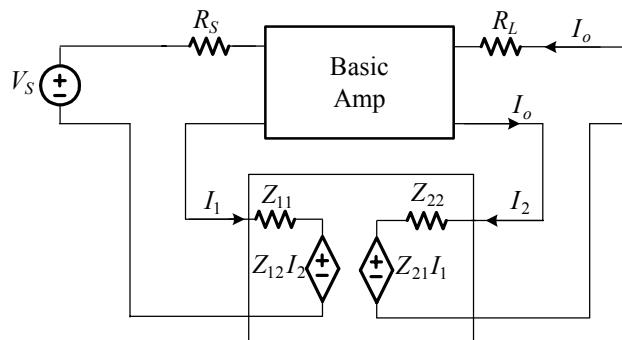

實際 β 網路

(b)以Z參數表示 β 網路

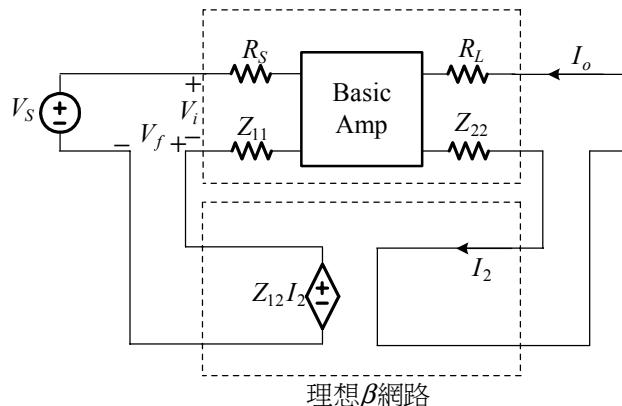


理想 β 網路

(c)轉換成理想模式（忽略 Z_{21} ）


圖10.19 實際串串回授放大器電路圖

【解題方法】


1. 基本放大器 A : 串串迴授

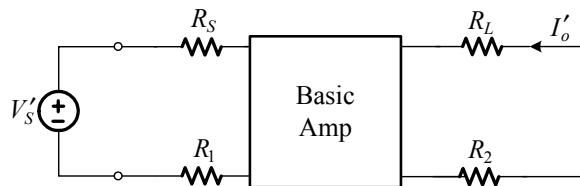輸入串聯 \Rightarrow 電壓訊號源 \Rightarrow 將輸入迴路化成戴維寧型式串聯 R_1 輸出串聯 \Rightarrow 電流輸出、電流取樣迴授 \Rightarrow 將輸出迴路串聯 R_2 

$$A = \frac{I'_o}{V'_s} \sim \text{互導增益}$$

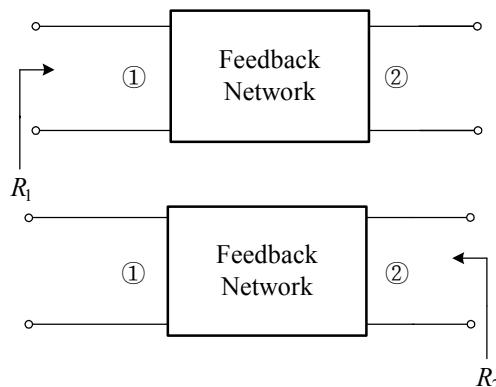2. 決定 R_1 及 R_2 :Series \Rightarrow 開路求 R_1 : 將②開路，由①看入求 R_2 : 將①開路，由②看入3. 決定 β :電流取樣 \Rightarrow ②端加上電流源 I'_o (與 I_o 同向)電壓混合 \Rightarrow ①端開路，量 V'_f

$$\beta = \left. \frac{V'_f}{I'_o} \right|_{I_1=0}$$

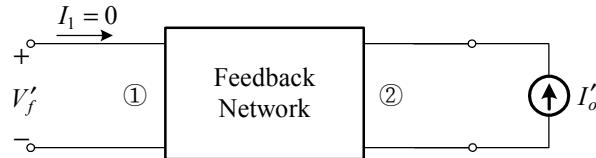

$$4. A_f = \frac{A}{1 + \beta A} \quad \dots \dots \dots \quad (10.16)$$

$$R'_{if} = (1 + A\beta)R_i \quad \dots \dots \dots \quad (10.17)$$

$$R'_{of} = (1 + A\beta)R_o \quad \dots \dots \dots \quad (10.18)$$

• 節題 10 •

Figure shows a voltage-controlled current-source circuit. It embodies feedback of the current-sampling series-mixing type. However, for practical reasons the current being sampled is not the output current in the collector but rather the almost equal emitter current. We wish to carry out small-signal analysis to determine I_o/V_s , R'_{if} , and R'_{of} .

